



Sanjay Ghodawat University, Kolhapur

2018-19

Established as State Private University under Govt. of Maharashtra. Act No XL, 2017 EXM/P/09/01

Year and Program: 2018-19

School of Technology

Department of Electrical Engineering

Course Code: ~~EET 208~~

Course Title: Power Electronics

Semester – IV

Day and Date: Tuesday,

End Semester Examination

Time: 10.30 am-1.30 pm

28/5/2019

(ESE)

Max Marks: 100

Instructions:

- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary.
- 3) Figures to the right indicate full marks.

Q.1	Solve any Two	Marks	Bloom's Level	CO
a)	Give comparison between MOSFET & IGBT	07	L ₃	CO1
	OR			
a)	Sketch and discuss briefly switching characteristics of thyristor during its turn on and turn off processes.	07	L ₃	CO1
b)	Describe the operation of a single phase two pulse full wave mid-point converter with relevant voltage and current waveforms. Discuss how each SCR is subjected to a reverse voltage equal to double the supply voltage in case turns ratio from primary to each secondary is unity. Find the circuits turn off time provided to each SCR by this converter configuration.	08	L ₃	CO2
	OR			
b)	Describe the operation of a three phase full wave full controlled bridge converter feeding power to R-L load by showing the waveforms of input line voltage, load voltage for a firing angle of 60°. Derive also expression for average load voltage.	08	L ₃	CO2
Q.2	Solve any Two			
a)	What is DC chopper? Describe the working of type A&C chopper with their waveforms	07	L ₂	CO3
	OR			
a)	Describe the principle of DC chopper operation. Derive an expression for its average output voltage	07	L ₂	CO3

ESE

Page 1/3

	b)	Describe the three phase to single phase cycloconverter feeding R-L load with output frequency one eighth of input frequency .Illustrate your answer by showing one cycle of low frequency output voltage.	08	L ₂	CO4
	OR				
	b)	Describe the basic principle of working of single phase to single phase step up cycloconverter with the help of bridge type configuration. Illustrate your answer with appropriate circuit and waveforms. The conduction of various thyristor must also be indicate on the waveforms.	08	L ₂	CO4
Q.3	Solve any Two				
	a)	Define string efficiency for series/parallel connected SCR'S .Show that string efficiency of two series connected SCR is usually less than one.	08	L ₃	CO1
	b)	For a single phase one pulse controlled converter system sketch waveforms for load voltage and load current for 1)R-L load and 2)R-L load with freewheeling diode across R.From a comparison of these waveforms discuss the advantages of using freewheeling diode.	08	L ₃	CO2
	c)	Sketch type B chopper. Does it operate as step down or step up chopper? Explain.	08	L ₃	CO3
	d)	Sketch the single phase to single phase step up cycloconverter with the help of midpoint type configuration. Organize your answer with appropriate circuit and waveforms. The conduction of various thyristor must also be indicate on the waveforms.	08	L ₃	CO4
Q.4	Solve any Two				
	a)	Describe the working of single phase full wave bridge inverter connected to inductive load. Draw the load voltage and load current waveforms. Also indicate the conduction of various elements of inverter circuit	09	L ₂	CO5
	b)	Discuss the principle of working of three phase bridge inverter. Draw the relevant waveform considering 120° mode of operation and star connected resistive load.	09	L ₂	CO5
	c)	Describe the working of single phase half wave bridge inverter connected to resistive load. Draw the load voltage and load current waveforms. Also indicate the conduction of various elements of	09	L ₂	CO5

inverter circuit.

Q.5

Solve any Two

- | | | | |
|--|----|----------------|-----|
| a) Analyze SMPS with a push pull configuration | 09 | L ₄ | CO6 |
| b) What is UPS? Give its industrial application. Describe and compare rotating type ,short break static type UPS configuration | 09 | L ₄ | CO6 |
| c) Describe and compare both types of HVDC links with relevant circuits. Derive equivalent circuit of a HVDC system. | 09 | L ₄ | CO6 |

Q.6

Solve any Three

- | | | | |
|--|----|----------------|-----|
| a) Explain in detail multiple pulse modulation techniques. | 06 | L ₂ | CO5 |
| b) Describe the working of single phase full wave bridge inverter connected to resistive load. Draw the load voltage and load current waveforms. Also indicate the conduction of various elements of inverter circuit. | 06 | L ₂ | CO5 |
| c) Describe a battery charger with a relevant circuit diagram. | 06 | L ₂ | CO6 |
| d) Explain the working of an emergency lighting system with suitable circuit diagram. | 06 | L ₂ | CO6 |

ESE

Page 3/3